

Md. Ishtiaq Ahamed Fahim  
2012518642

Task-1

**C.2. Procedure**

Input Reference	$A B C$	$F$	Min term	Max term
0	0 0 0	0		
1	0 0 1	1		
2	0 1 0	1		
3	0 1 1	0		
4	1 0 0	0		
5	1 0 1	0		
6	1 1 0	1		
7	1 1 1	0		

**Table C.1 Truth table to a combinational circuit**

1. Write down all the min terms and max terms of three inputs  $ABC$  in Table C.1.
2. Write down the function  $F$  in 1<sup>st</sup> and 2<sup>nd</sup> Canonical Forms in Table C.2.

	Shorthand Notation	Function
1 <sup>st</sup> Canonical Form	$F = \Sigma$	$F =$
2 <sup>nd</sup> Canonical Form	$F = \Pi$	$F =$

**Table C.2 1<sup>st</sup> and 2<sup>nd</sup> canonical forms of the combinational circuit of Table C.1**



Table:

# Task - 1

Input Reference	ABC	F	min term	Max term
0	0 0 0	0	$A'B'C'$	$A+BC$
1	0 0 1	1	$A'B'C$	$A+B+C'$
2	0 1 0	1	$A'BC'$	$A+B'+C$
3	0 1 1	0	$A'BC$	$A+B+C'$
4	1 0 0	0	$AB'C'$	$A'+B+C$
5	1 0 1	0	$AB'C$	$A'+B+C'$
6	1 1 0	1	$AB'C'$	$A'+B'+C$
7	1 1 1	0	$ABC'$	$A'+B'+C'$

	Short hand Notation	function
1st Canonical Form	$F = \sum (1, 2, 6)$	$F = A'B'C + A'BC' + ABC'$
2nd Canonical form	$F = \prod (0, 3, 4, 5, 7)$	$F = (A+BC)(A+B'+C)(A'+B+C)(A'+B'+C)$

Logisim:

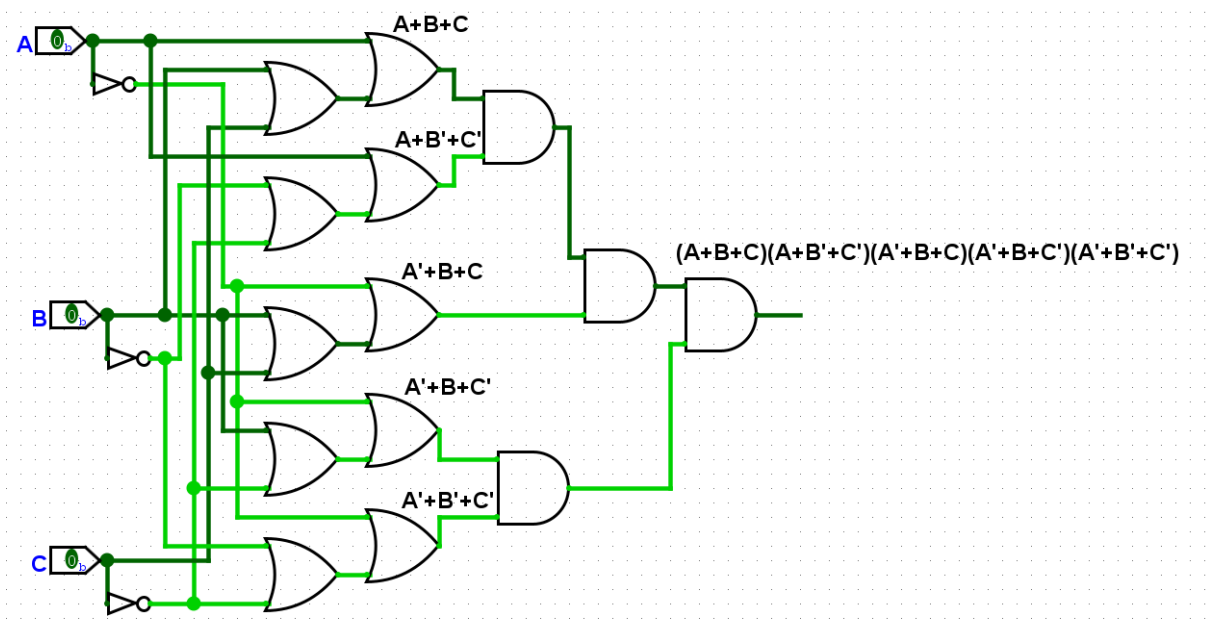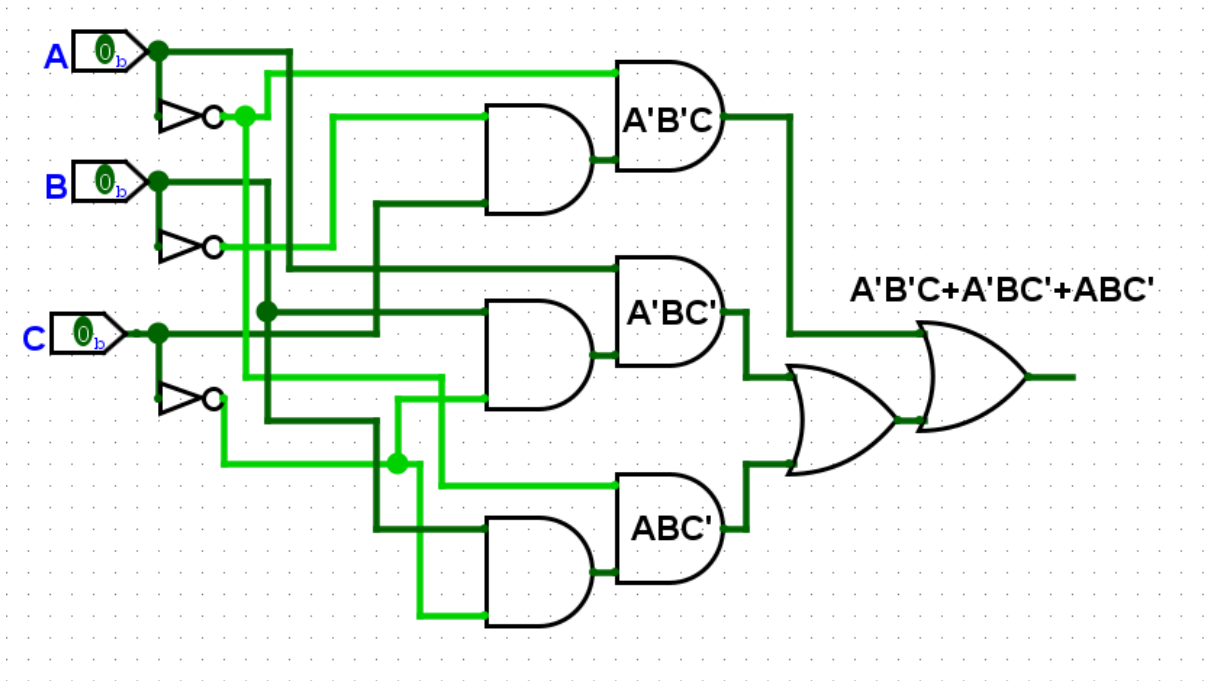

Task-2

D.2. Procedure

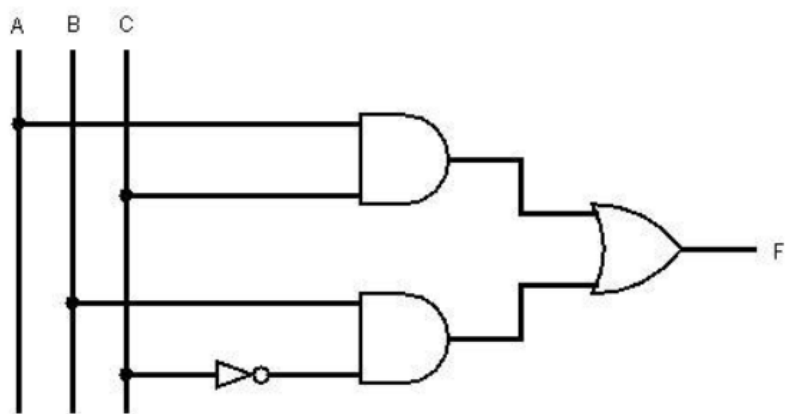


Figure 0.1 A combinational circuit

1. Complete the truth table for the circuit of Figure 0.1 in Table 0.1.

<i>XYZ</i>	<i>I<sub>1</sub> = AC</i>	<i>I<sub>1</sub> = BC'</i>	<i>F</i>
0 0 0			
0 0 1			
0 1 0			
0 1 1			
1 0 0			
1 0 1			
1 1 0			
1 1 1			

Table 0.1 Truth table of the combination circuit of Figure 0.1

Table:

# Task-2

A	B	C	$I_2 = \overline{A}B\overline{C}$	$I_1 = \overline{A}\overline{B}C$	$F = I_1 + I_2$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	0	1	1
1	1	1	1	0	1

	ABC	F	Min term	Max term
0	0 0 0	0		$\overline{A} + \overline{B} + \overline{C}$
1	0 0 1	0		$\overline{A} + \overline{B} + C$
2	0 1 0	1	$\overline{A} \cdot B \cdot \overline{C}$	$\overline{A} + B + \overline{C}$
3	0 1 1	0		$\overline{A} + B + C$
4	1 0 0	0	$A \cdot \overline{B} \cdot \overline{C}$	
5	1 0 1	1	$A \cdot \overline{B} \cdot C$	
6	1 1 0	1	$A \cdot B \cdot \overline{C}$	
7	1 1 1		$A \cdot B \cdot C$	

1st canonical form

Short hand notation  
 $F = \Sigma(2, 5, 6, 7)$

function  
 $F = \overline{A}B\overline{C} + A\overline{B}C + ABC + A\overline{B}\overline{C}$

2nd canonical form

$F = \Pi(0, 1, 3, 4)$

$F = (\overline{A} + \overline{B} + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + B + C) \cdot (A + \overline{B} + \overline{C})$

Logisim:

